

# Electronics Night: Basic AC Analysis


(slides will **not** be a regular feature)

# Capacitor: current leads voltage by 90 degrees


$$V(t) = \sqrt{2} \sin(2\pi t) \text{ V} \quad (1\text{V-rms})$$

$$C = 0.2\text{F}$$


$$I(t) = C \frac{dV(t)}{dt}$$

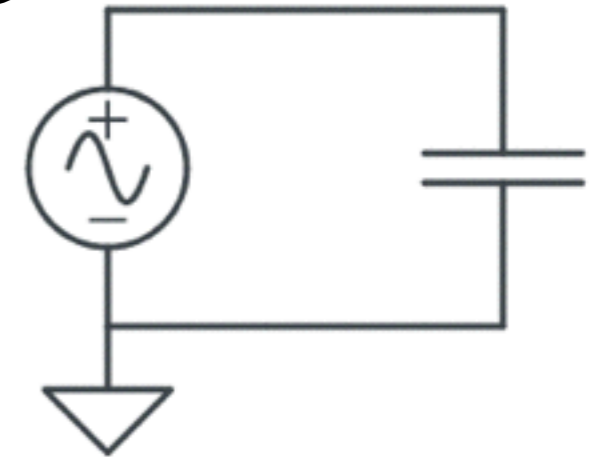
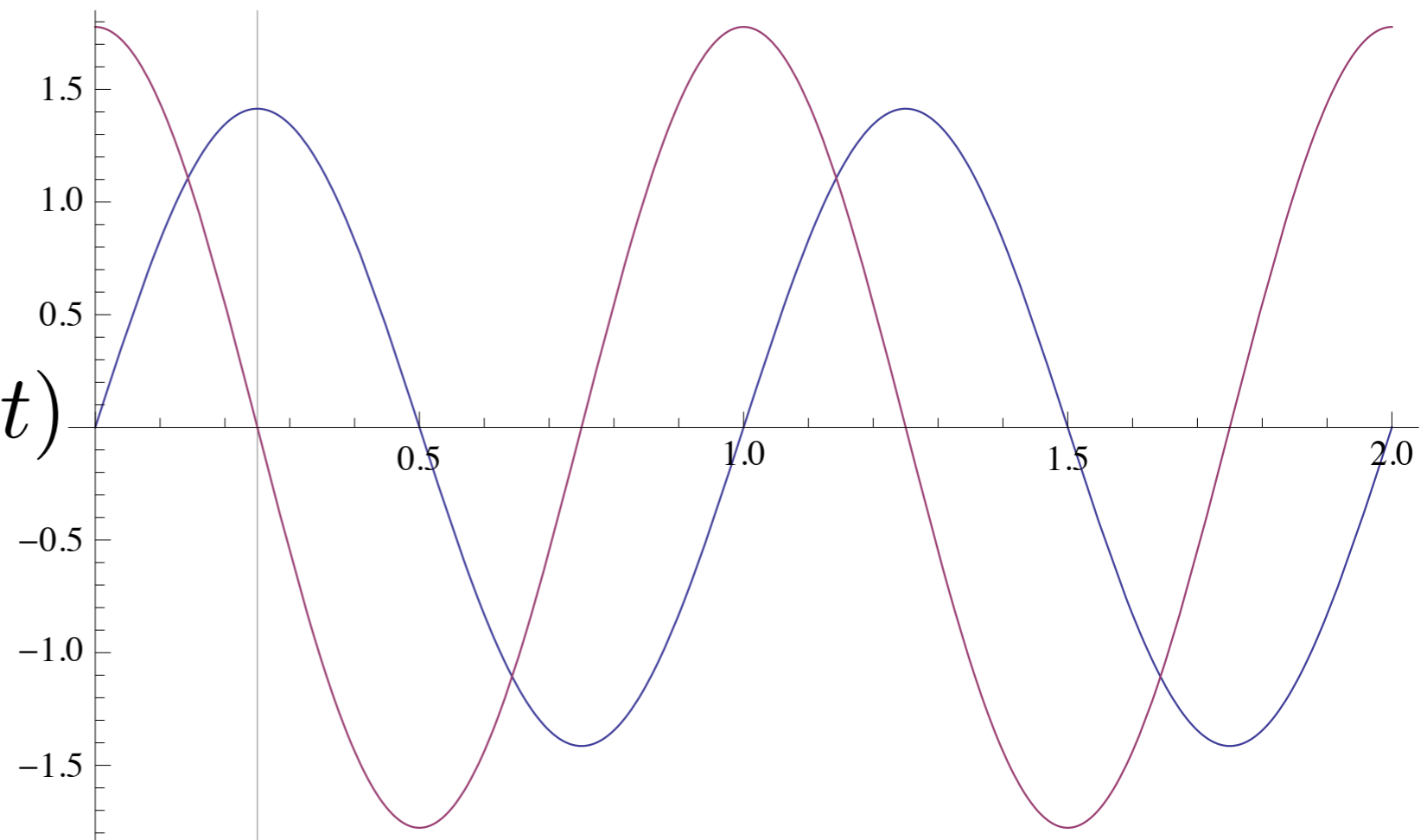
$$\frac{dV(t)}{dt} = 2\sqrt{2}\pi \cos(2\pi t)$$




A capacitor resists **changes in voltage** by storing energy in an electric field

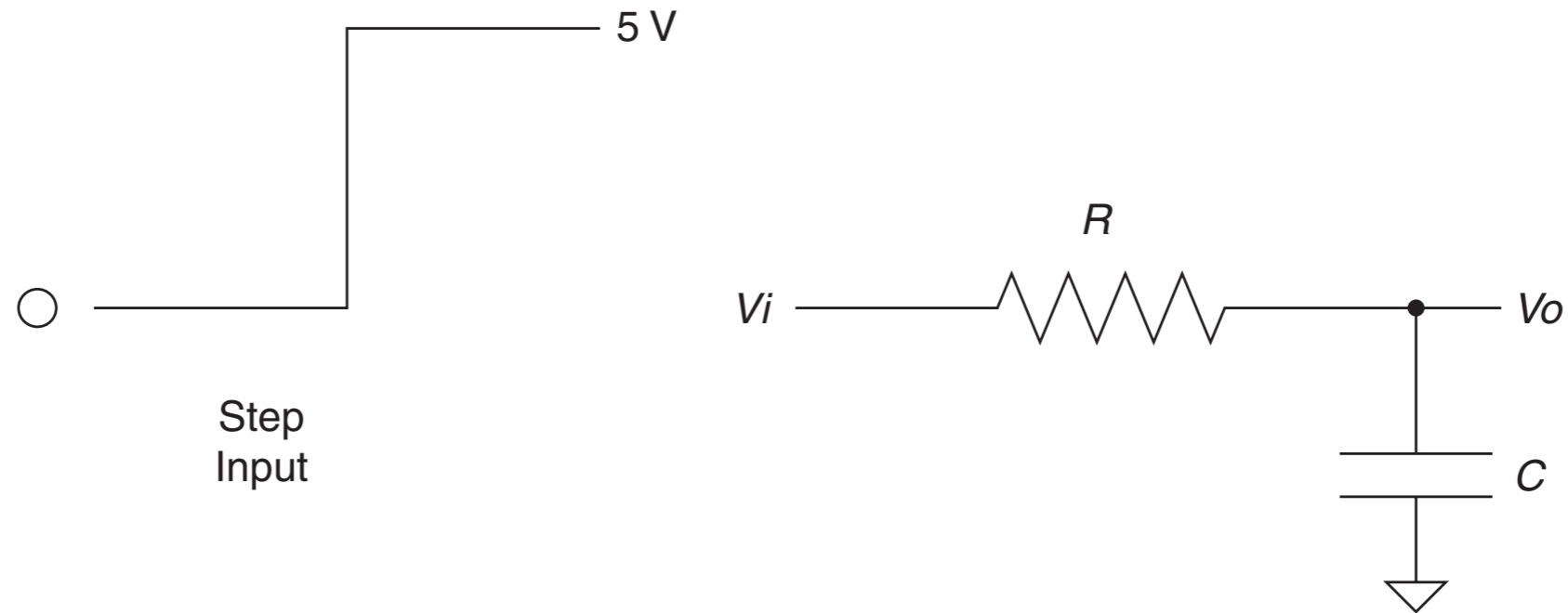

**FIGURE 2.6**

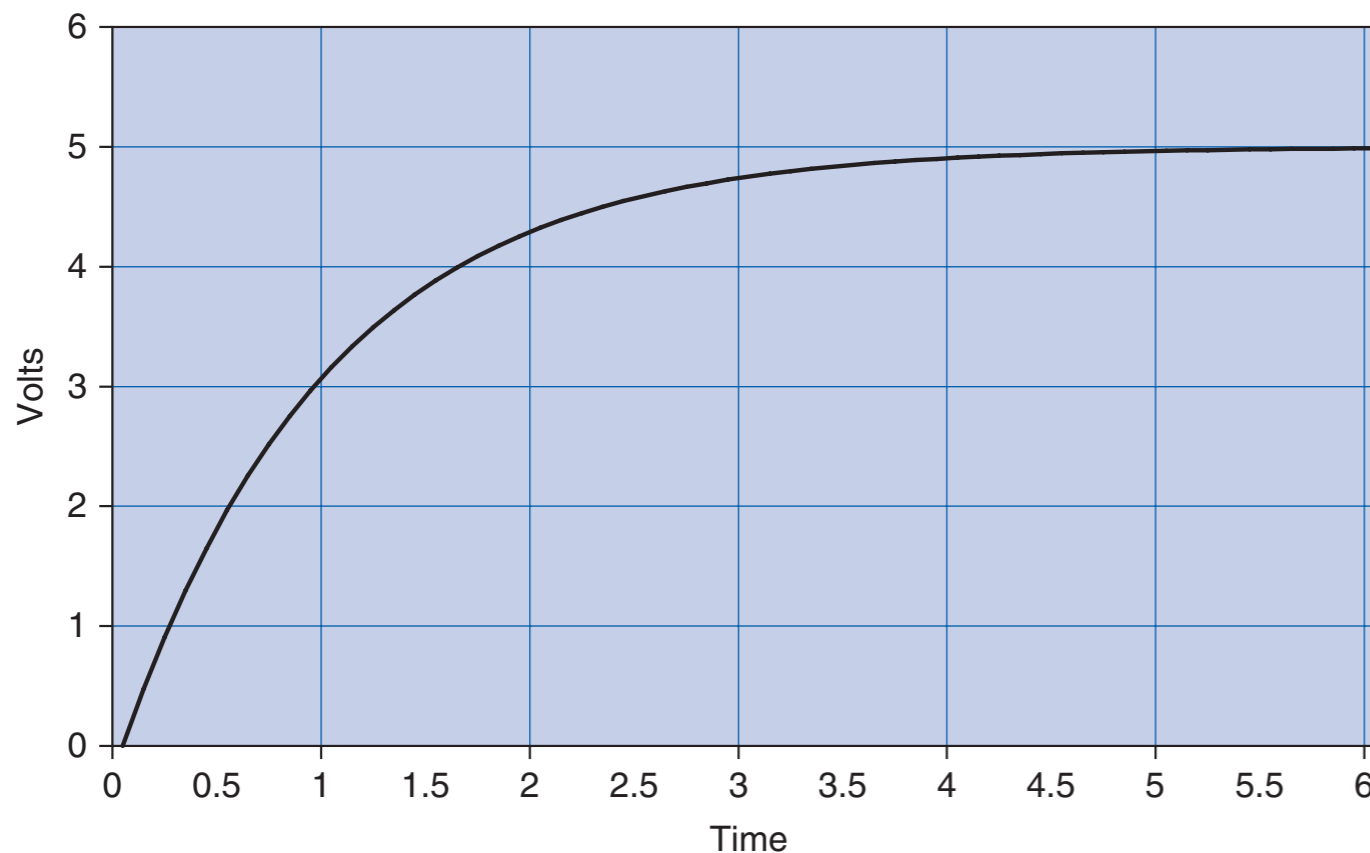
Step input is applied to a simple RC circuit.



$$V_o = V_i \left( 1 - e^{-\frac{\tau}{rc}} \right)$$

Reaches 63% of steady state voltage in one time constant

An inductor resists **changes in current** by storing energy in a magnetic field

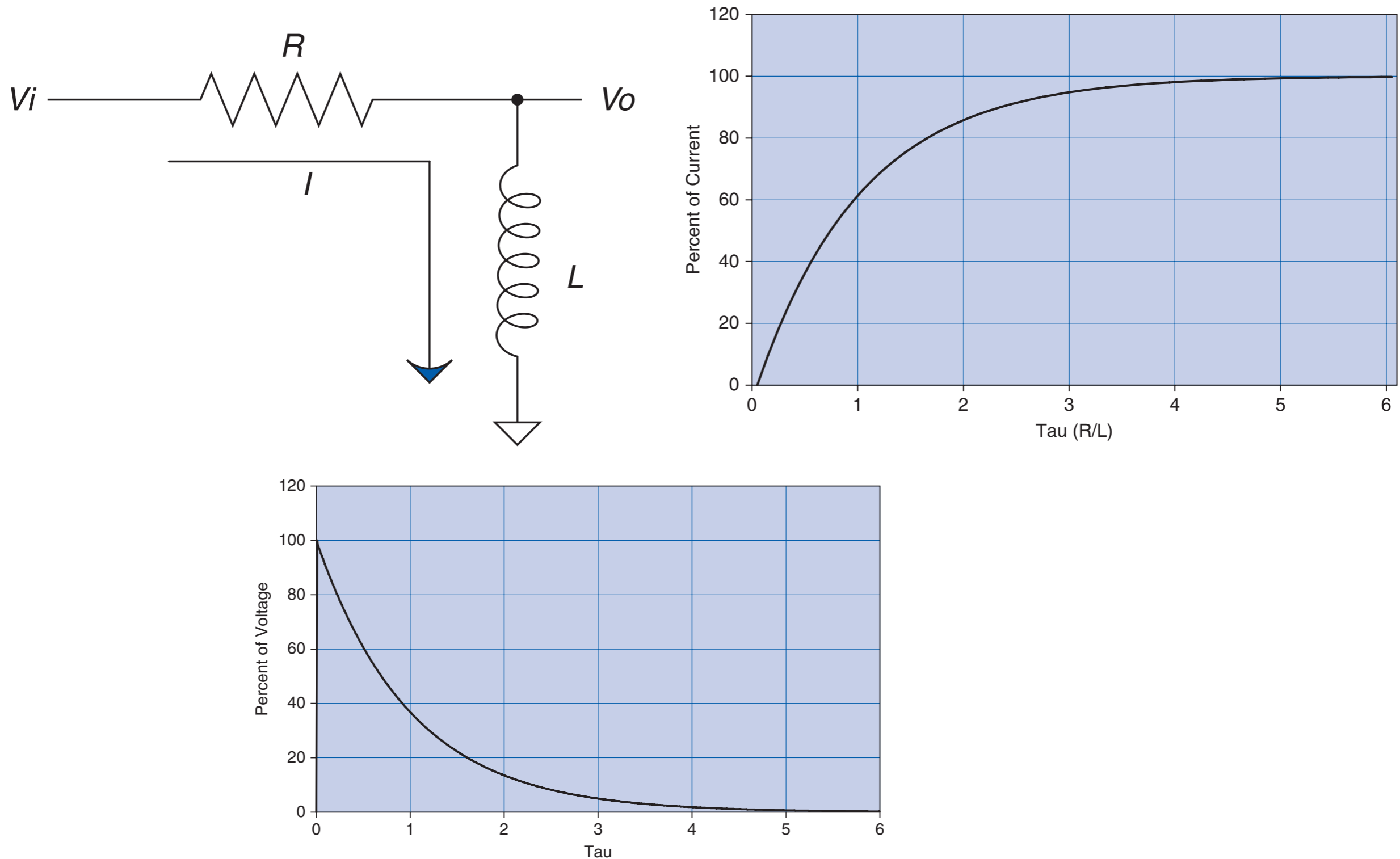


**FIGURE 2.12**  
Voltage change in percent over time in tau.


# Reactance

$$X_c = \frac{1}{2\pi f C}$$

$$X_L = 2\pi f L$$

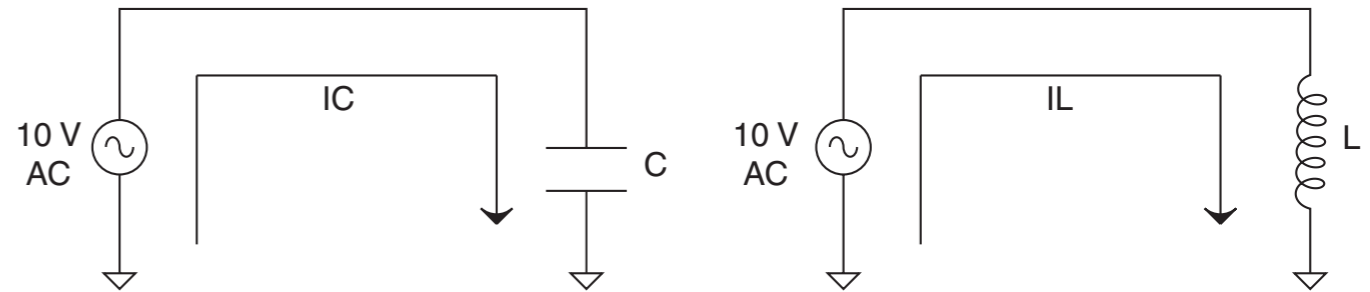


**FIGURE 2.30**  
AC source hooked up to cap and inductor.

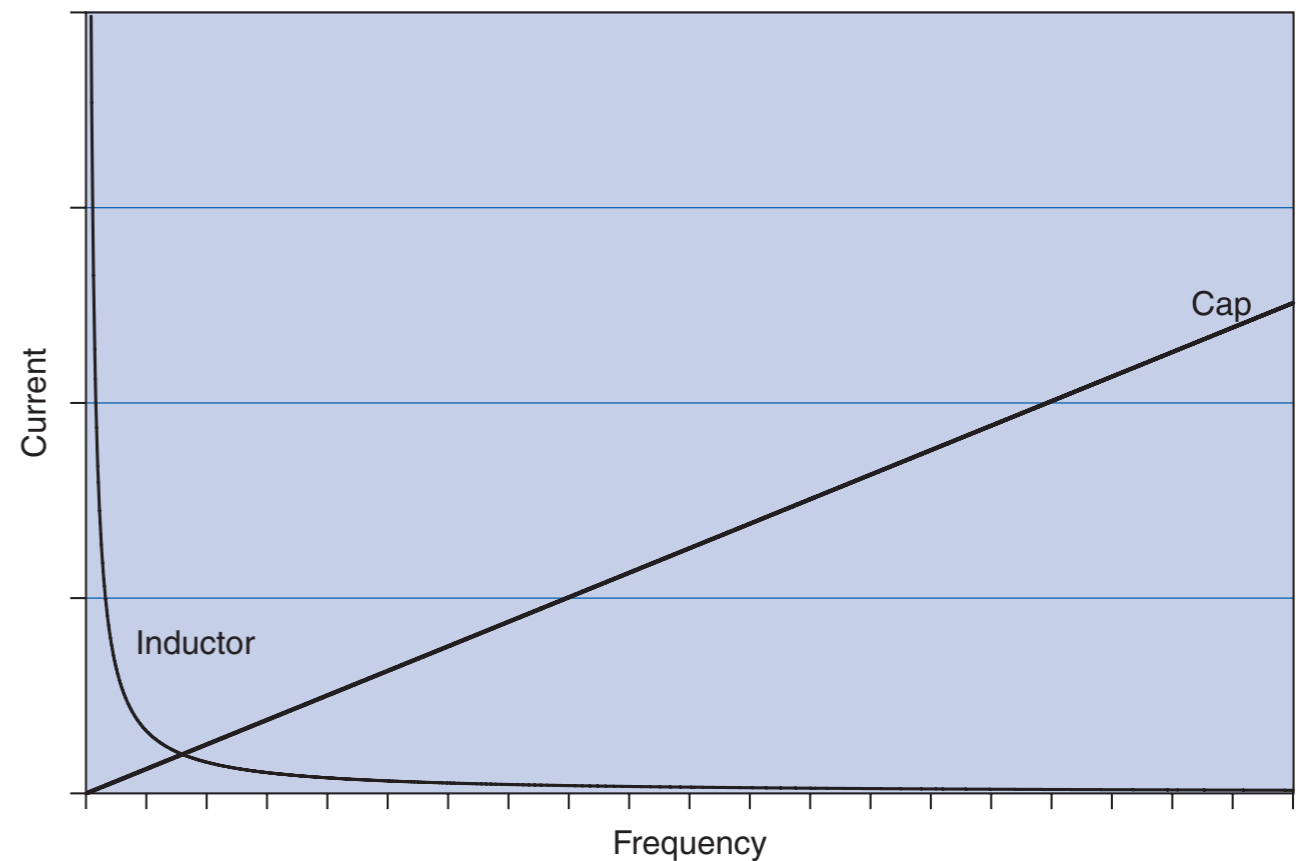

**FIGURE 2.31**  
Graph of current over frequency for a cap and an inductor.
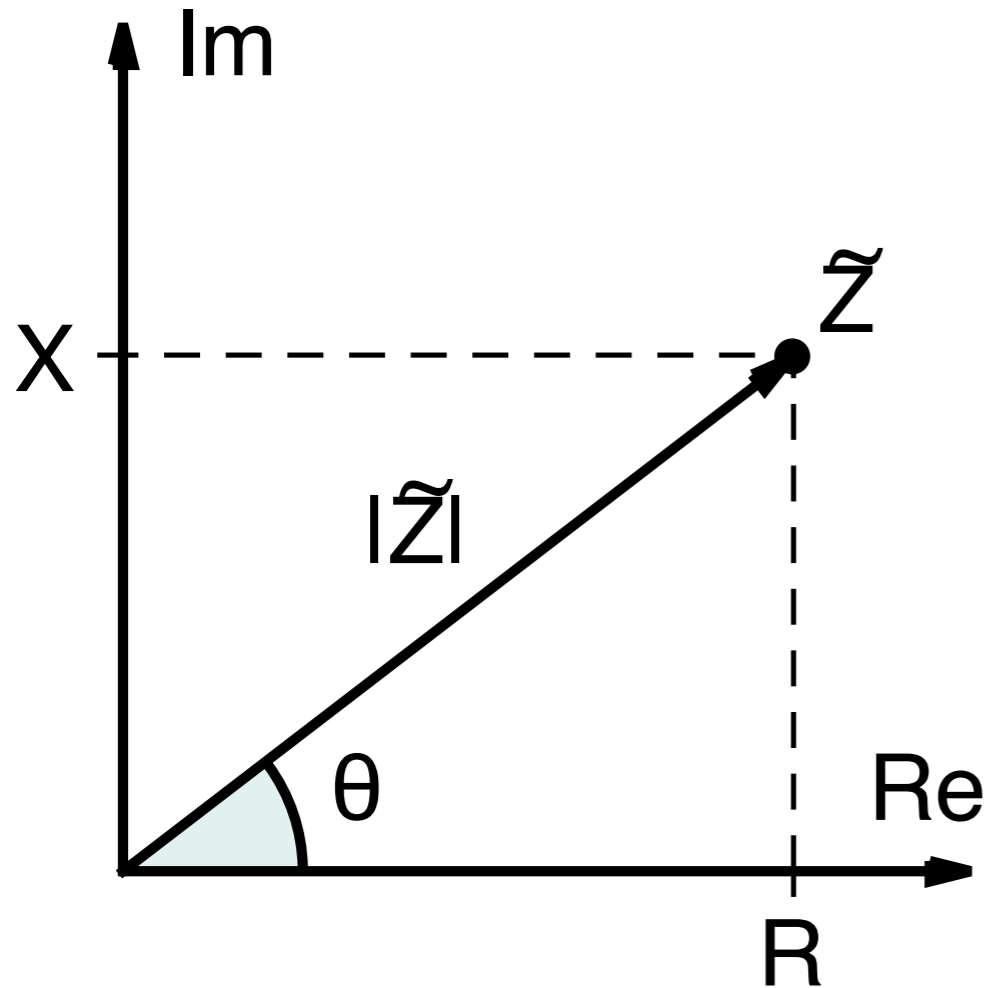
# Impedance




Real part: **resistance**

Imaginary part: **reactance**

Magnitude: **voltage/current**

Angle: voltage **phase shift**

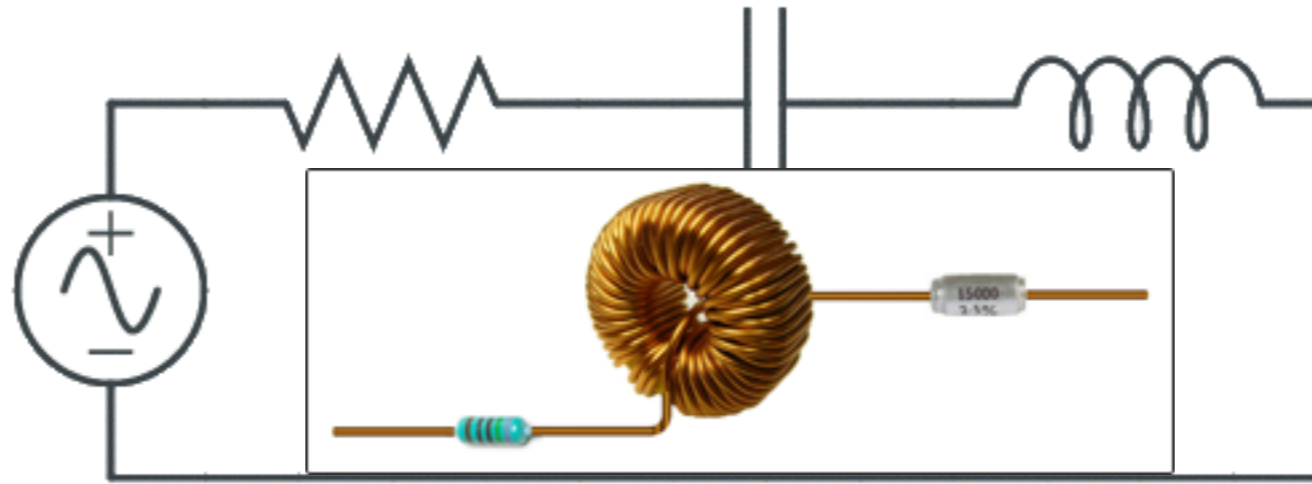
This is essentially **frequency domain analysis**



$$X_C = 500 \, \Omega, \quad R = 1 \, \text{k}\Omega, \quad X_L = 250 \, \Omega$$

$$X = X_L - X_C = -250 \, \Omega$$

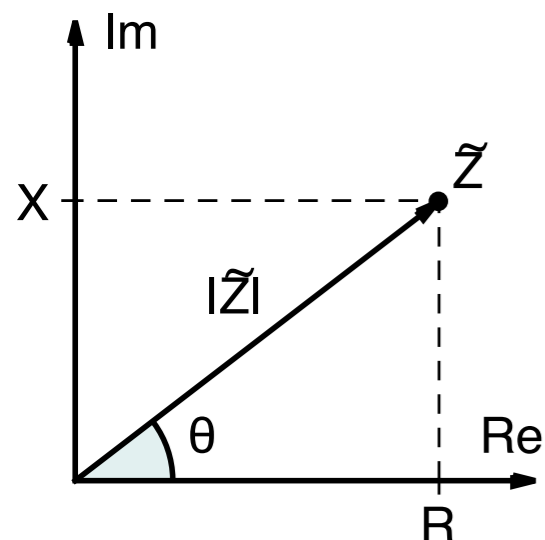
$$\theta = -\sin^{-1}(250/1000) = -14^\circ$$



Voltage lagging current 14 degrees

Depends on frequency!

# Resonance

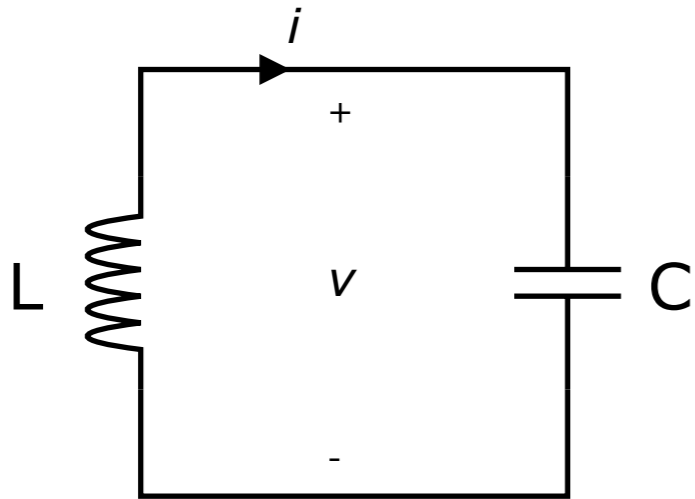

At the resonant frequency,  
capacitive reactance equals  
inductive reactance

$$2\pi f L = \frac{1}{2\pi f C}$$


$$f = \frac{1}{2\pi \sqrt{LC}}$$


# Example

The resonant frequency of a series RLC circuit if R is 22 ohms, L is 50 microhenrys and C is 40 picofarads is 3.56 MHz. (E5A14)

$$f = 1/2\pi\sqrt{LC} = 1/6.28\sqrt{(50\times 10^{-6} \times 40\times 10^{-12})} = 1/2.8\times 10^{-7} = \mathbf{3.56 \text{ MHz}}$$

# General solution method

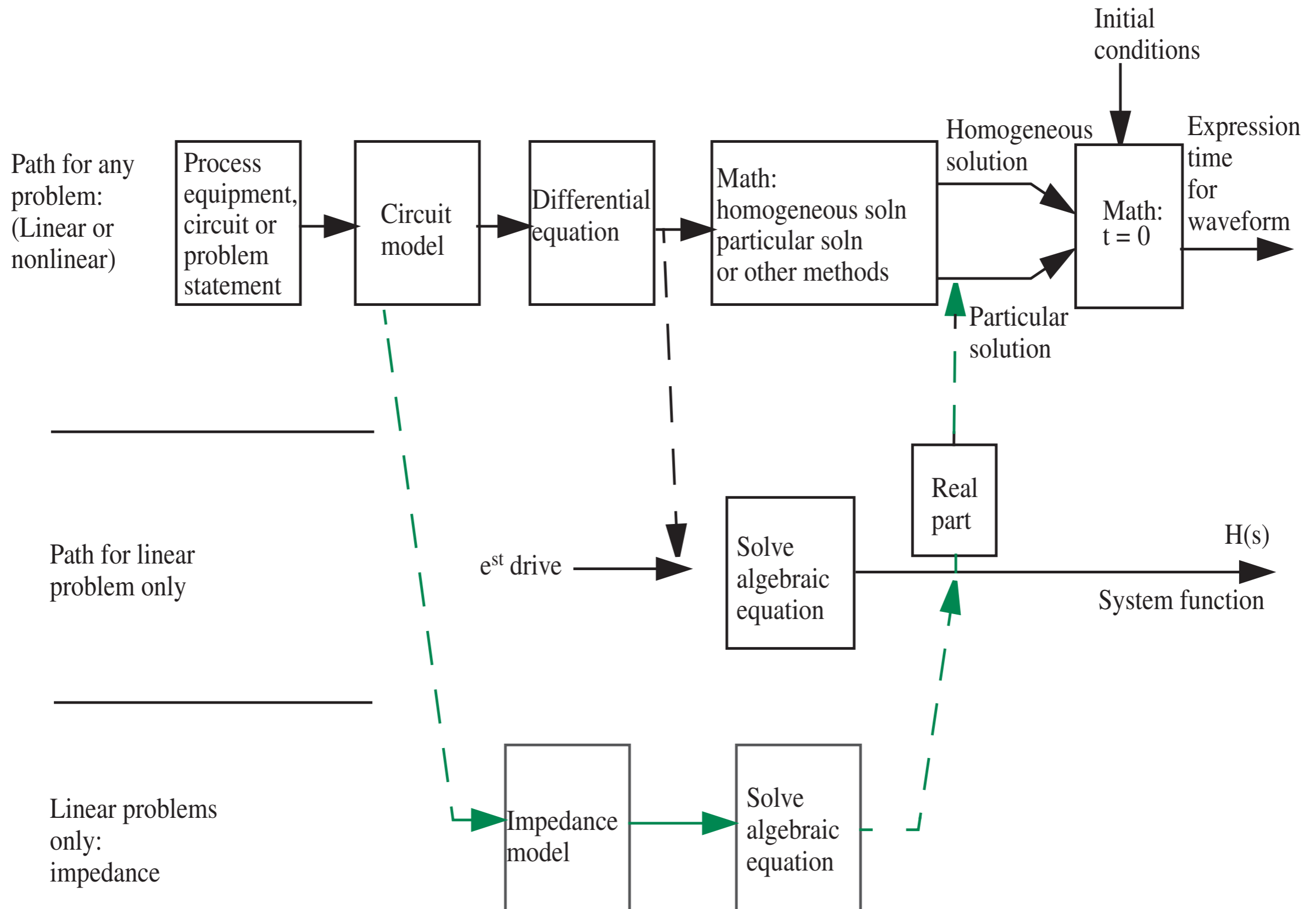

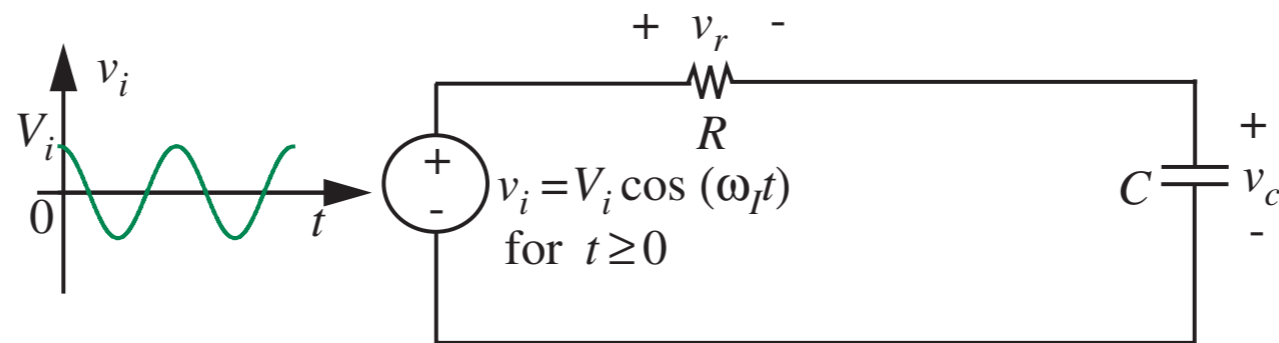

$$v_i = V_i \cos(\omega_1 t) \quad \text{for } t \geq 0,$$

$$v_i = v_c + RC \frac{dv_c}{dt}.$$

Homogenous  
solution:

$$RC \frac{dv_{ch}}{dt} + v_{ch} = 0. \quad v_{ch} = K_1 e^{-t/RC}$$

Particular  
solution:


$$\tilde{v}_{cp} = \frac{V_i}{1 + j\omega_1 RC} e^{j\omega_1 t}. \quad e^{i\omega t} = \cos(\omega t) + i \sin(\omega t)$$

Complete solution  
(steady state):


$$v_c = \frac{V_i}{\sqrt{1 + (\omega_1 RC)^2}} \cos(\omega_1 t + \Phi)$$

$$v_c \simeq \frac{V_i}{\omega_1 RC} \cos(\omega_1 t - 90^\circ)$$


# Filters

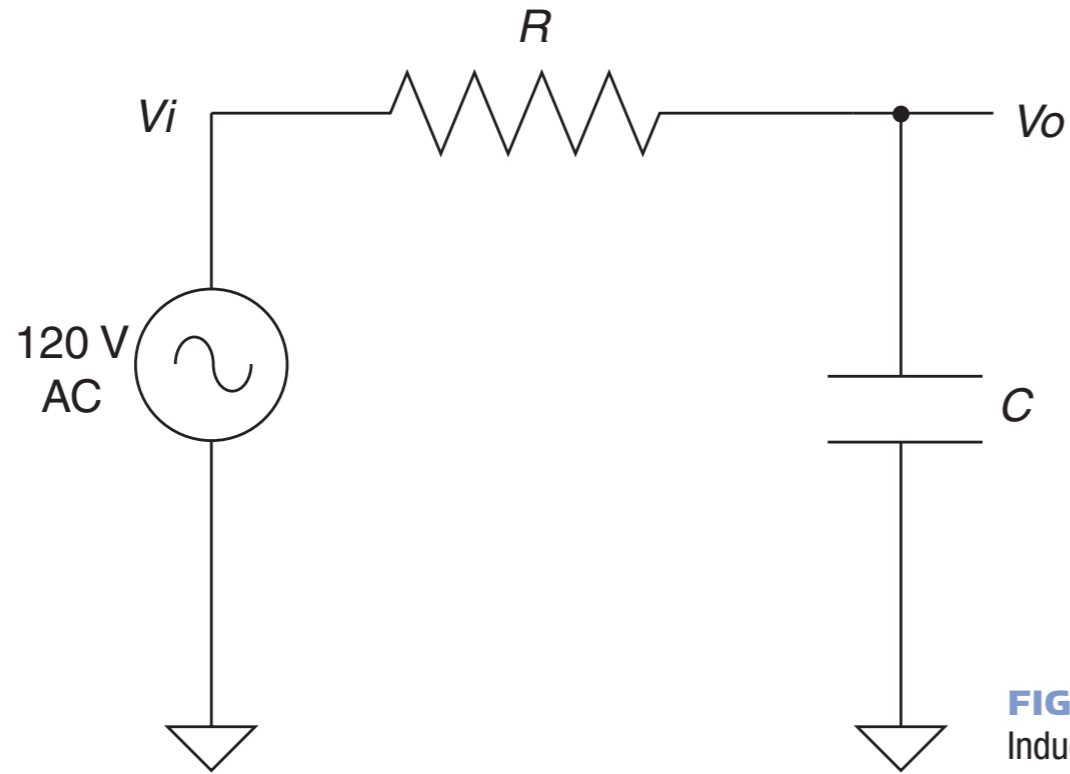

**FIGURE 2.32**  
Cap-based low-pass filter.

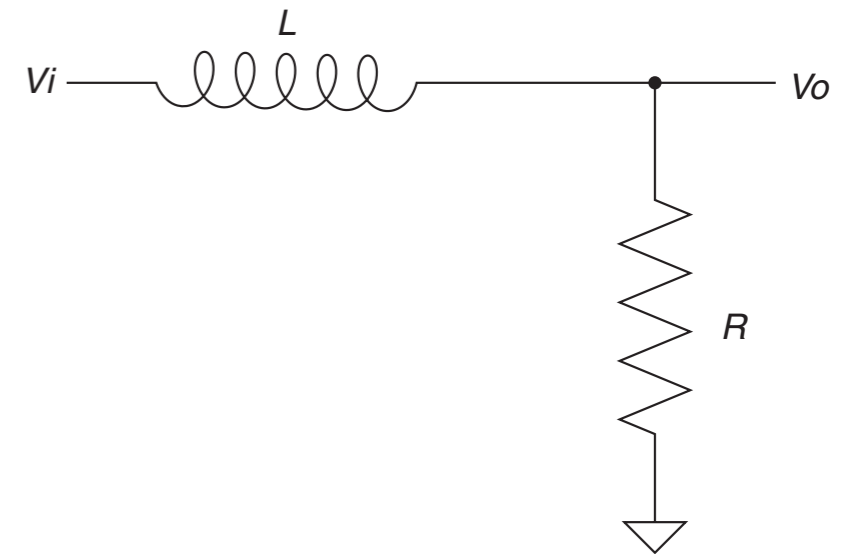


**FIGURE 2.33**  
Inductor-based low-pass filter.

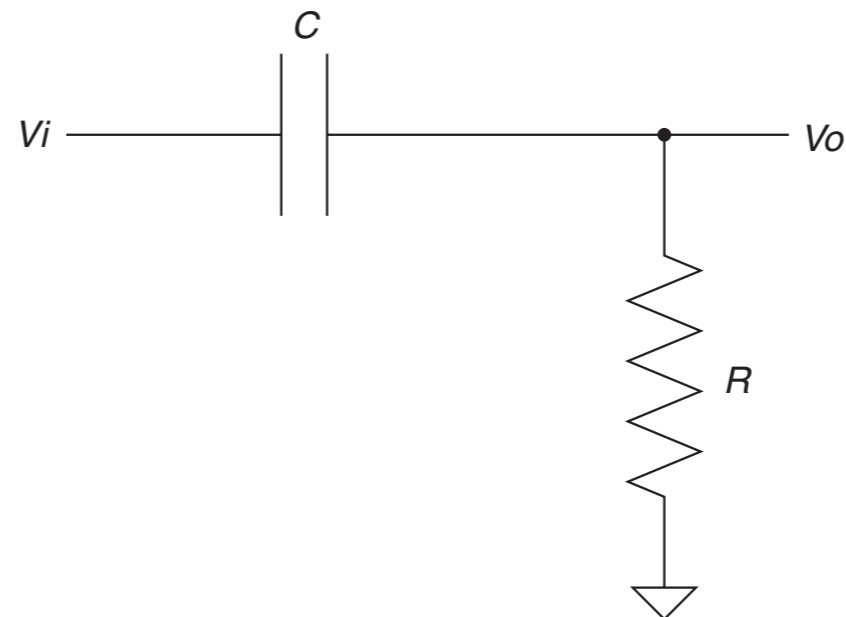


**FIGURE 2.34**  
Cap-based high-pass filter.
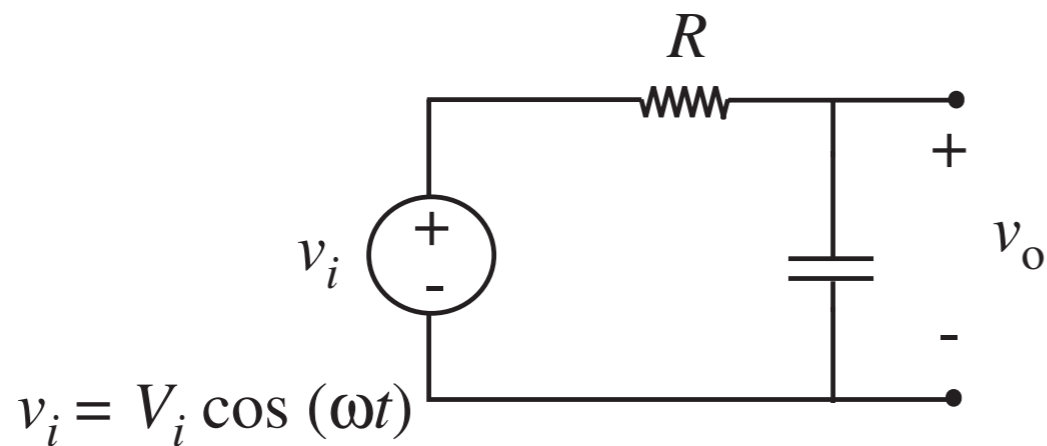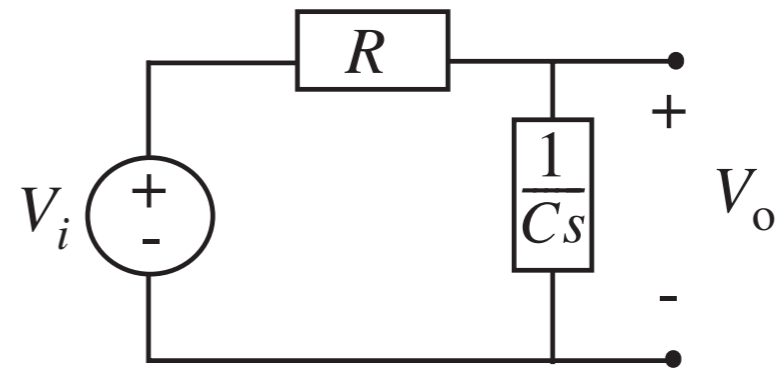
# Low pass RC filter



(a) Circuit



(b) Impedance model

( $s$  is shorthand for  $2i\pi f$ )

Voltage divider:

$$V_o = \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} V_i = \frac{1/RC}{s + 1/RC} V_i$$

Gain:

$$H(2i\pi f) = \frac{V_o}{V_i} = \frac{1/RC}{2i\pi f + 1/RC}$$

What happens at low frequencies?  
What happens at high frequencies?

